

19U509S

(Pages: 2)

Name:

Reg. No:

FIFTH SEMESTER B.Sc. DEGREE EXAMINATION, NOVEMBER 2021

(CUCBCSS-UG)

CC15U PH5 B09 - ELECTRONICS (ANALOG & DIGITAL)

(Physics – Core Course)

(2015 to 2018 Admissions – Supplementary/Improvement)

Time: Three Hours

Maximum: 80 Marks

SECTION A

Answer *all* questions. Each question carries 1 mark.

1. The ripple factor of a full wave rectifier is
2. A Zener diode is in bias for voltage regulation
3. State De-Morgan's theorems.
4. What is the point of intersection of d c and a c load lines?
5. $(F2.C4)_{16} = ()_8 = ()_2$

True or False:

6. In an A M, majority of power is in side bands.
7. All binary numbers cannot be converted to decimal numbers.
8. Octal is not a positional number system.
9. The electrical equivalent of mass is capacitance.
10. A transistor is a current operated device.

(10 × 1 = 10 Marks)

SECTION B

Answer *all* questions. Each question carries 2 marks.

11. What is the need of modulation?
12. Explain the terms, decibel power gain and frequency response.
13. Convert the decimal 54 to binary.
14. Explain the working of a voltage doubler.
15. Draw the circuit diagram of common base configuration.
16. What is Faithfull amplification? How can we achieve it?
17. What are the main differences between A M and F M?

(7 × 2 = 14 Marks)

SECTION C

Answer any *five* questions. Each question carries 4 marks.

18. Explain the working of a full wave rectifier.
19. What is thermal runaway? Write a short note on stabilization of operating point of transistor amplifier.

20. Discuss the function of transformer in a transformer coupled amplifier.
21. explain the working of J K flipflop.
22. Explain the working of MOSFET.
23. Draw the circuit diagram of a Hartley oscillator.
24. Mention the truth tables of half adder and full adder.

(5 × 4 = 20 Marks)

SECTION D

Answer any *four* questions. Each question carries 4 marks.

25. A 6 V Zener diode is connected with a voltage source of 10 V and a resistance R. The current through the load resistance R_L varies from 10 to 100 mA. Find the value of series resistance R for maintaining a voltage of 7 V across R_L . The minimum Zener current is 8 mA.
26. Subtract 9 from 15 using 2's complement method in 8 bit format.
27. A JFET has $I_{DSS} = 9 \text{ mA}$, $V_{GS(\text{off})} = -6 \text{ V}$. Find the value of drain current when $V_{GS} = -3 \text{ V}$.
28. Explain, with truth tables, the logic gates NOR, NAND and XOR. Why NAND and NOR gates are called universal gates?
29. Obtain the simplified SOP forms of the function $F(A,B,C,D) = \Sigma (0,1,2,5,8,9,10)$ using K-MAP
30. Draw the d c load line for CE configuration having $V_{CC} = 10\text{V}$, $R_C = 5\text{k}\Omega$. What will be the Q Point if zero signal base current is $15\mu\text{A}$?
31. After amplitude modulation, the r.m.s value of carrier wave changes from 80V to 65V. Calculate the modulation index.

(4 × 4 = 16 Marks)

SECTION E

Answer any *two* questions. Each question carries 10 marks.

32. What are the advantages of OP-AMP? Explain the working of OP-AMP as 1) summing amplifier 2) integrator and 3) differentiator.
33. What are the essentials of a transistor oscillator? Discuss the working of 1) Hartley oscillator 2) crystal oscillator.
34. With a neat diagram, explain the working of a two stage RC coupled amplifier.
35. Explain with neat diagram the working of a full wave rectifier. Derive an expression for its efficiency

(2 × 10 = 20 Marks)
