

24U208

(Pages: 2)

Name : .....

Reg. No : .....

**SECOND SEMESTER UG DEGREE EXAMINATION, APRIL 2025**

(FYUGP)

**CC24UPHY2MN100 - ELECTRONICS - I**

(Physics - Minor Course)

(2024 Admission -Regular)

Time: 2.0 Hours

Maximum: 70 Marks

Credit: 4

**Part A** (Short answer questions)

Answer *all* questions. Each question carries 3 marks.

1. Discuss the working principle of a LED with diagram. [Level:2] [CO3]
2. Discuss different factors affect the breakdown voltage of a diode? [Level:2] [CO2]
3. Differentiate between half-wave, full-wave, and bridge rectifiers based on efficiency. [Level:4] [CO3]
4. Compare the output frequency of a half-wave rectifier to that of a full-wave rectifier. [Level:4] [CO3]
5. Express the formula for collector-emitter voltage (VCE) in voltage divider bias. [Level:2] [CO4]
6. Explain the power rating of a transistor. [Level:2] [CO4]
7. Define an analog signal and a digital signal. [Level:1] [CO6]
8. Identify the decimal equivalent of the BCD number 1001 0001. [Level:1] [CO6]
9. Convert the decimal number 25 into hexadecimal. [Level:1] [CO6]
10. Mention the binary equivalent of the decimal number 64. [Level:1] [CO6]

**(Ceiling: 24 Marks)**

**Part B** (Paragraph questions/Problem)

Answer *all* questions. Each question carries 6 marks.

11. Calculate the conductivity of an intrinsic semiconductor given the following data: [Level:1] [CO1]  
electron mobility  $\mu_e = 0.14 \text{ m}^2/V$ , hole mobility  $\mu_h = 0.05 \text{ m}^2/V$  and  
intrinsic carrier concentration  $n_i = 1.5 \times 10^{16} \text{ m}^{-3}$ . (The electronic charge  
 $e = 1.6 \times 10^{-19} \text{ C}$ .)
12. The reverse saturation current ( $I_s$ ) of a PN junction diode is 5 nA at room [Level:1] [CO1]  
temperature. If the thermal voltage ( $V_T$ ) is 26 mV, calculate the forward current

(If) when the diode is forward biased with 0.3 V.

13. A full wave rectifier uses two diodes , the internal resistance of each diode may be assumed as constant at  $20 \Omega$ . The transformer rms secondary voltage from centre tap to each end of secondary is 50 V and load resistance is  $980 \Omega$ . Compare mean load current and rms value of load current. [Level:4] [CO3]
14. Analyze the differences in output stability between center-tapped and half wave rectifiers. [Level:4] [CO3]
15. Discuss the biasing with collector feedback circuit. [Level:2] [CO4]
16. Discuss the working principles of n-p-n and p-n-p transistors based on charge carrier movement. [Level:2] [CO4]
17. Find and discuss the relationship between current amplification factors in CB and CC arrangement in transistor connection. [Level:2] [CO4]
18. Name the place values of the digits in the binary number 10110. Then, write its decimal equivalent. [Level:1] [CO6]

**(Ceiling: 36 Marks)**

**Part C (Essay questions)**

Answer any *one* question. The question carries 10 marks.

19. Examine current paths in voltage doublers by considering the circuit action. [Level:4] [CO3]
20. Explain the concept of faithful amplification in a transistor and analyse its importance in transistor biasing. Illustrate how improper biasing affects faithful amplification. [Level:2] [CO4]

**(1 × 10 = 10 Marks)**

\*\*\*\*\*